 



大哥哥大姊姊講半導體

4

認識積體電路-邏輯閘





大哥哥大姊姊講半導體

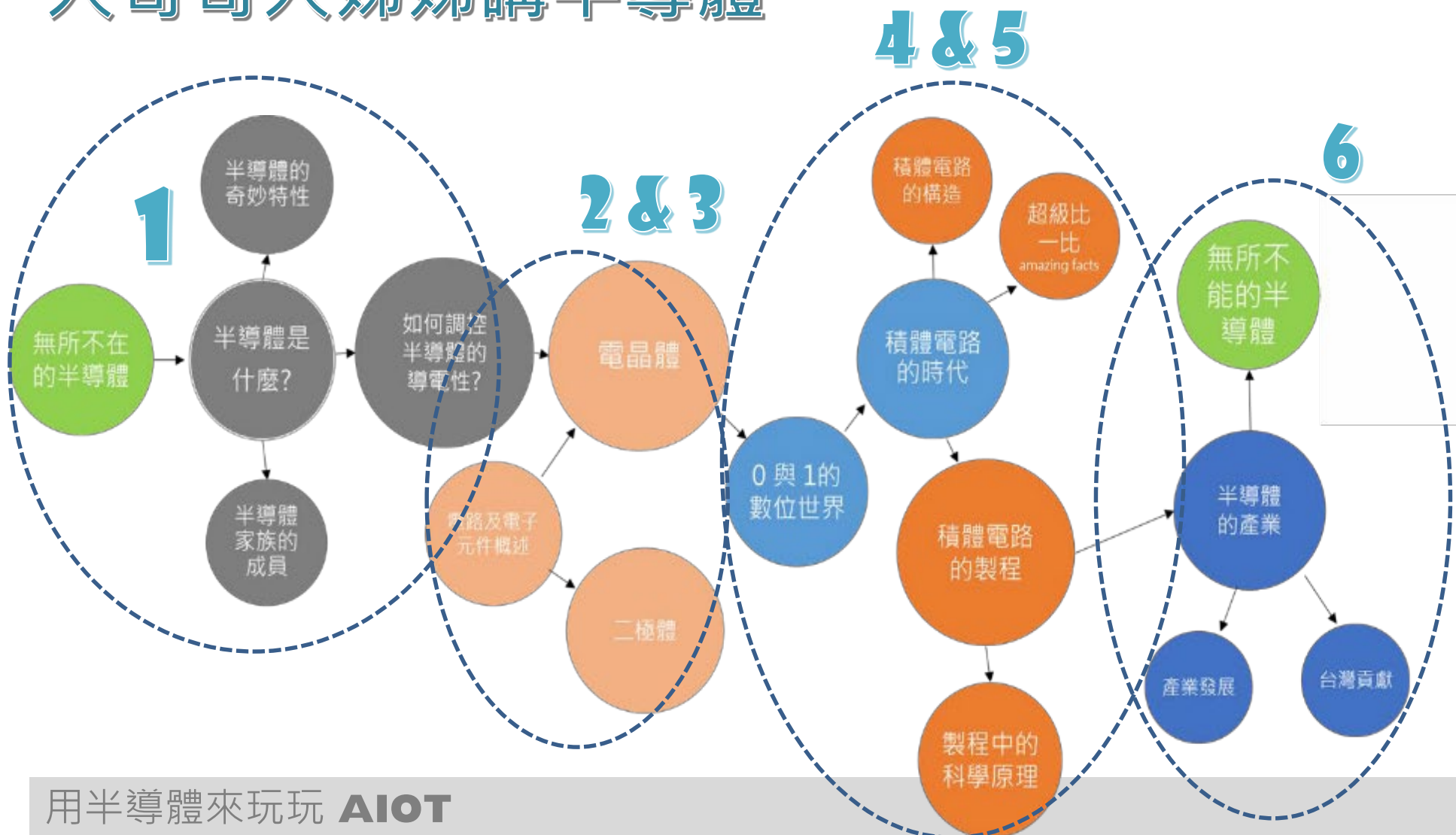


用半導體來玩玩 AIOT

積體電路(Integrated Circuit)

  
- 積體電路(IC)為利用大量電晶體(Transistor)組成特定功能的元件。
 - 跟指頭一樣小的晶片上就有上億個電晶體。
- 為什麼要積體，如同居住在城市，房子密集發展為更有效運用空間



晶圓(round wafer)

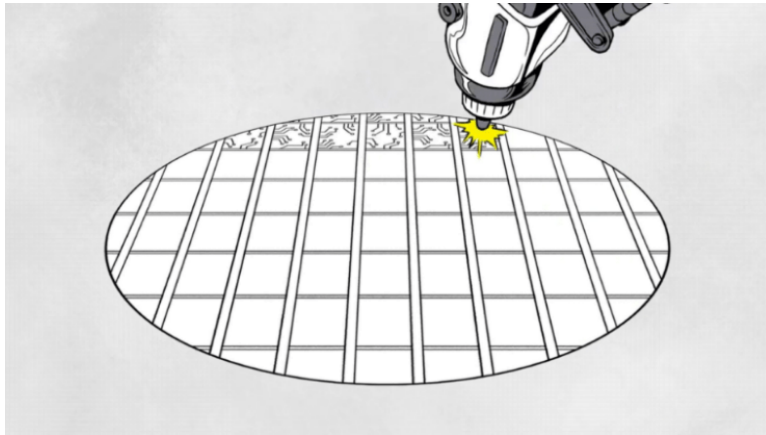

滿滿的電晶體!

 

10奈米有多小?

頭髮直徑約50微米，細菌的大小約1微米，病毒的大小約100奈米，而人類現在的技術能夠做出只有病毒1/10大小的結構!


電晶體的大小越小，電子在其中流動的所需的距離就越小、功耗越低、速度也就越快!

當電晶體變得更小，我們在同一塊晶圓上能夠塞下的電晶體就會變得更多!



更多的電晶體，更低的生產成本，我們買電子設備時，就能享受更優惠的價格!

數位 vs. 類比 Digital vs. Analog

- 類比訊號: 連續性型式進行傳遞, 並為數位訊號最終呈現方式。

 

- 數位訊號: 以0、1的非連續方式傳遞、運算及儲存。

  

數位訊號怎樣呈現

- 最基礎的數位訊號表達方式為0與1，就如同路上看到路燈不亮(0)與亮(1)
- 回家時怎麼跟家人明確說那些路燈不亮?



每個路燈有亮與不亮兩種狀態，依序表達

(狀態)² (狀態)¹ (狀態)⁰ => 假設第二根沒亮

1 0 1 (二進制表達: 101)

$1 * (2)^2 + 0 * (2)^1 + 1 * (2)^0 = 4 + 0 + 1 = 5$ (十進制表達)

IC晶片種類

- 邏輯晶片

- 執行OR、AND這類邏輯的晶片，讓輸入訊號給出相對應的輸出。



- 類比晶片

- 用於處理連續性的訊號，擁有耐高壓、耐高電流的特性。




- 記憶體晶片

- 儲存資料供日後需要資料時可以讀取。





- 微元件晶片

- 統合數據並進行計算，如電腦的CPU。

 


什麼是數位訊號的1與0

  - 訊號的1與0是依定義的電壓水準做判斷。
 - 讀訊號時超過定義1的電壓即為1。
 - 讀訊號時低於定義0的電壓即為0。



 

用電晶體，二極體，
 電阻及電容完成
Logic gates





Basic Digital Logic Gates


INPUT		OUTPUT
A	B	
0	0	0
1	0	0
0	1	0
1	1	1



 AND



 NAND

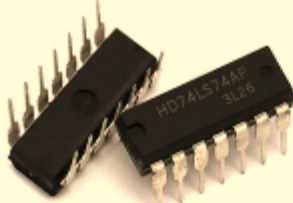

 OR


 NOR



 NOT


 XOR

 

 XNOR



A AND B	$A \cdot B$
A OR B	$A + B$
NOT A	\bar{A}
A XOR B	$A \oplus B$





用NAND Gate 組合成加法器
 用加法器組合加減乘除
 用加減乘除完成積分微分矩陣運算……
 用積分微分矩陣運算去完成 ……



或 (or gate)

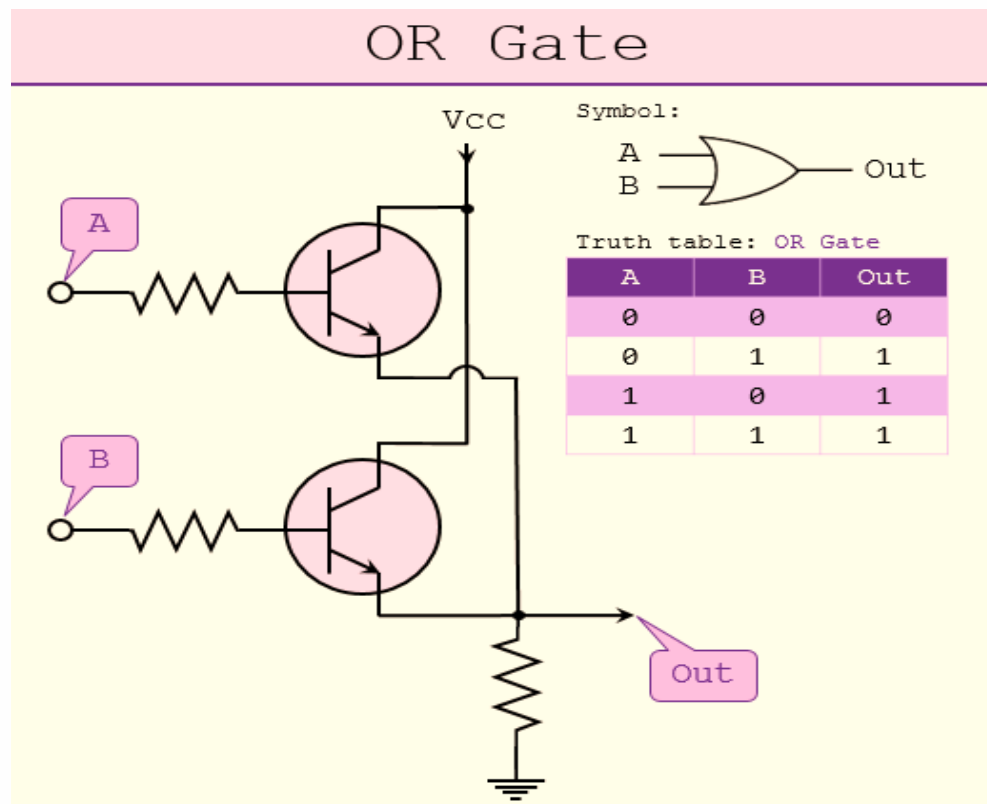
 
- OR gate輸出訊號，由多個輸入訊號組成，其中一個輸入訊號為1，輸出訊號就是1
- 如同要到校上課，每人走一條吊橋，只要其中有一條吊橋可通過(1)，就有人到校(1)。






且 (and) 邏輯閘

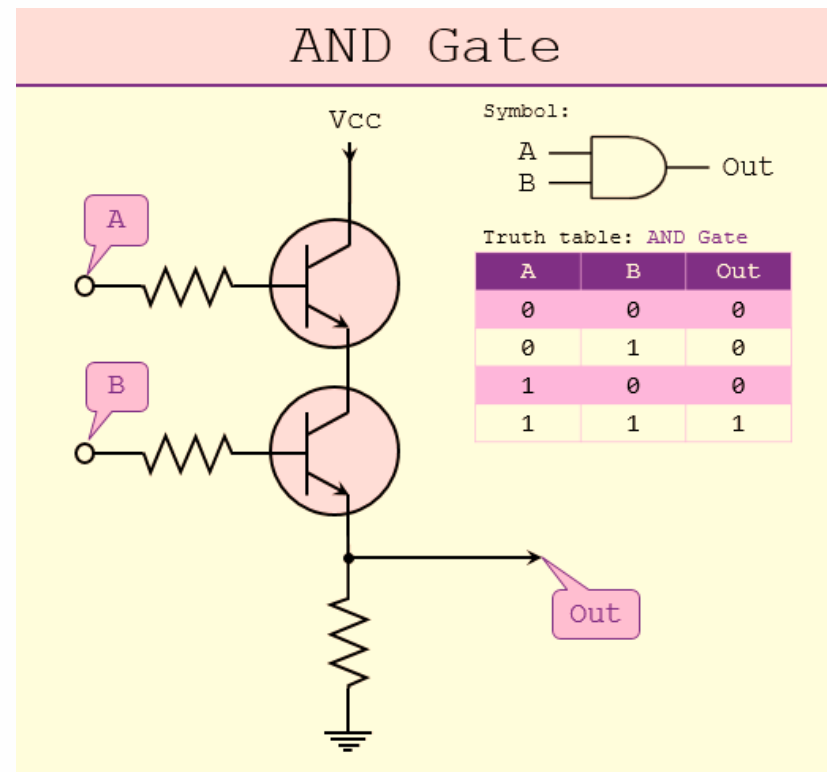 - AND gate 輸出訊號由多個輸入訊號組成，只要其中一個輸入訊號為 0，其輸出結果就是 0。
- 如同有人到校須經過一條由多段吊橋所組成的吊橋，只要其中一條吊橋無法通過 (0)，就無法到校 (0)。



反相器 (Not)

 


- 一個電路訊號，經反相器後輸出訊號與輸入訊號相反。
- 如同經過十字路口，當所在的馬路是綠燈時，則另一條路就會是紅燈，反之亦然。



NOT Gate


Symbol:

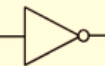A —  — Out

Truth table: NOT Gate

A	Out
0	1
1	0


輸入	輸出
0	1
1	0

 


XOR



A	B	Out
0	0	0
0	1	1
1	0	1
1	1	0

 

XNOR

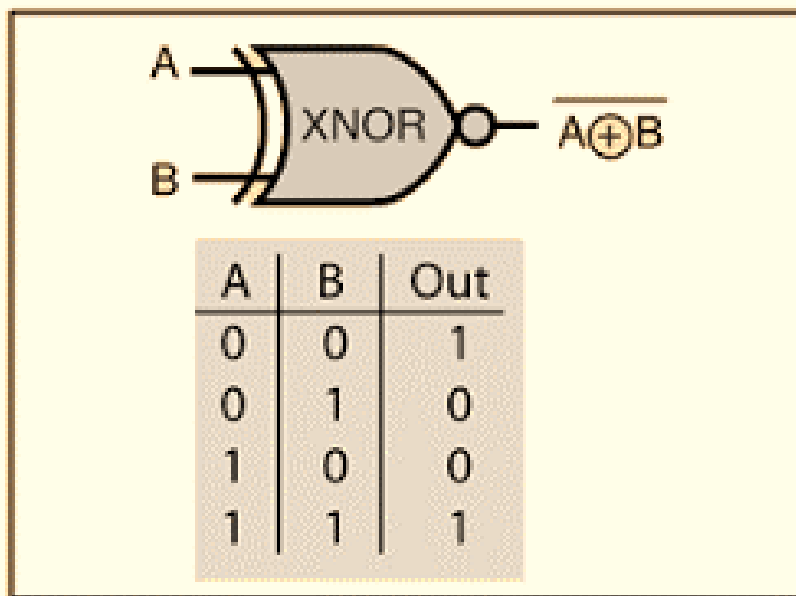


A	B	Out
0	0	1
0	1	0
1	0	0
1	1	1




7486

VCC

 

GND

Data Sheet

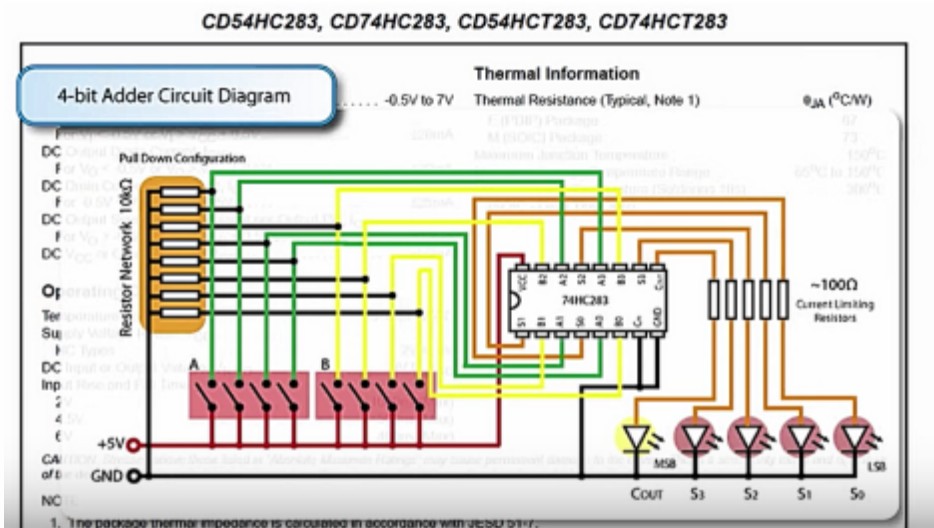

[CD54HC283, CD74HC283, CD54HCT283, CD74HCT283 datasheet \(Rev. D\) \(ti.com\)](http://www.ti.com)



Data sheet acquired from Harris Semiconductor
SCH5175D

November 1997 - Revised October 2003

CD54HC283, CD74HC283, CD54HCT283, CD74HCT283

High-Speed CMOS Logic 4-Bit Binary Full Adder with Fast Carry

Features

- Adds Two Binary Numbers
- Full Internal Lookahead
- Fast Ripple Carry for Economical Expansion
- Operates with Both Positive and Negative Logic
- Fanout (Over Temperature Range)
 - Standard Outputs 10 LSTTL Loads
 - Bus Driver Outputs 15 LSTTL Loads
- Wide Operating Temperature Range . . . -55°C to 125°C
- Balanced Propagation Delay and Transition Times
- Significant Power Reduction Compared to LSTTL Logic ICs
- HC Types
 - 2V to 6V Operation
 - High Noise Immunity: $N_{IL} = 30\%$, $N_{IH} = 30\%$ of V_{CC} at $V_{CC} = 5V$
- HCT Types
 - 4.5V to 5.5V Operation
 - Direct LSTTL Input Logic Compatibility, $V_{IL} = 0.8V$ (Max), $V_{IH} = 2V$ (Min)
 - CMOS Input Compatibility, $I_i < 1\mu A$ at V_{OL} , V_{OH}

Description

The 'HC283 and 'HCT283 binary full adders add two 4-bit binary numbers and generate a carry-out bit if the sum exceeds 15.

Because of the symmetry of the add function, this device can be used with either all active-high operands (positive logic) or with all active-low operands (negative logic). When using positive logic the carry-in input must be tied low if there is no carry-in.

Ordering Information

PART NUMBER	TEMP. RANGE (°C)	PACKAGE
CD54HC283F3A	-55 to 125	16 Ld CERDIP
CD54HCT283F3A	-55 to 125	16 Ld CERDIP
CD74HC283M	-55 to 125	16 Ld PDIP
CD74HCT283M	-55 to 125	16 Ld SOIC
CD74HC283MT	-55 to 125	16 Ld SOIC
CD74HCT283MT	-55 to 125	16 Ld SOIC
CD74HC283M95	-55 to 125	16 Ld SOIC
CD74HCT283M95	-55 to 125	16 Ld SOIC





NOTE: When ordering, use the entire part number. The suffix 96 denotes tape and reel. The suffix T denotes a small-quantity reel of 250.



$Q = A \text{ NAND } B$

Truth Table

Input A	Input B	Output Q
0	0	1
0	1	1
1	0	1
1	1	0

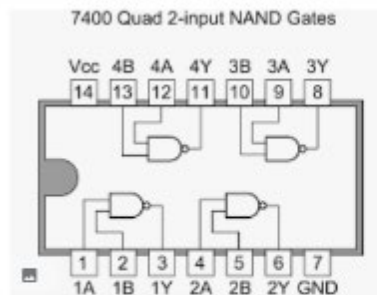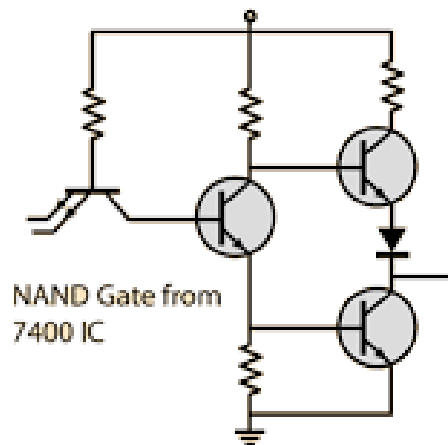 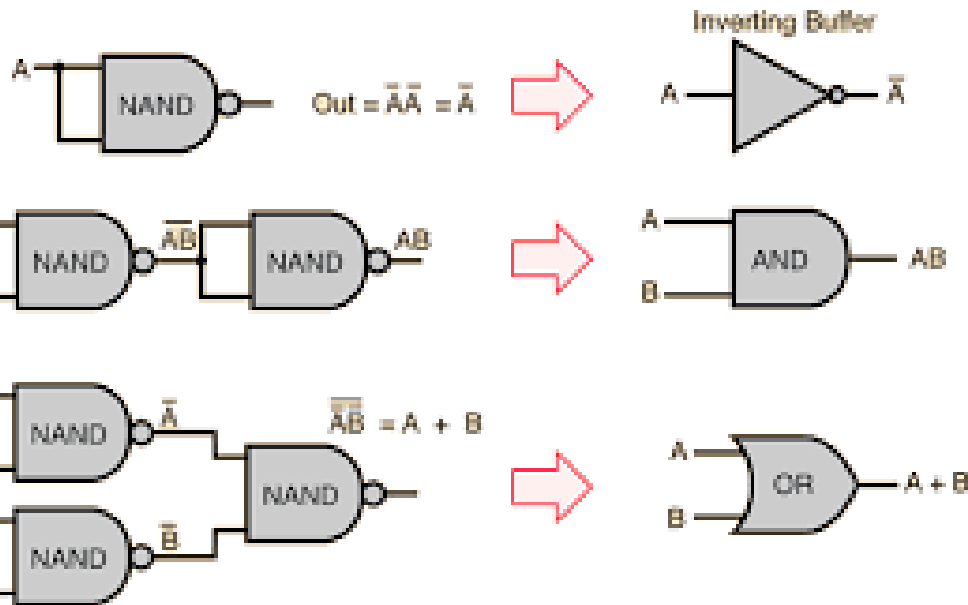

File:7400 Quad 2-input NAND Gates.PN... commons.wikimedia.org



JRe'S 7400 ic NAND gate (set of 5 pcs) : Amazon... amazon.in

Binary

- Example: Base 10 number (Decimal)

- $(123.456)_{10} = 1 \times 10^2 + 2 \times 10^1 + 3 \times 10^0 + 4 \times 10^{-1} + 5 \times 10^{-2} + 6 \times 10^{-3}$



The subscripts indicate “base-10 numeral system”

- Example: **Base 2 number (Binary)**

- $(101.101)_2 = 1 \times 2^2 + 0 \times 2^1 + 1 \times 2^0 + 1 \times 2^{-1} + 0 \times 2^{-2} + 1 \times 2^{-3}$

- Example: Base 8 number (Octal)

- $(101.101)_8 = 1 \times 8^2 + 0 \times 8^1 + 1 \times 8^0 + 1 \times 8^{-1} + 0 \times 8^{-2} + 1 \times 8^{-3}$

- Example: Base 16 number (Hexadecimal)

- $(101.101)_{16} = 1 \times 16^2 + 0 \times 16^1 + 1 \times 16^0 + 1 \times 16^{-1} + 0 \times 16^{-2} + 1 \times 16^{-3}$

Integer Number to Base-R Number Conversion

- 10進位整數轉2進位
 - 不斷地除以2，直到結果為0
 - 得到的餘數就是結果
- Example: $53_{10} \rightarrow$ Binary number

Convert 53_{10} to binary.

$$\begin{array}{r} 2 \overline{) 53} \\ 2 \overline{) 26} \quad \text{rem.} = 1 = a_0 \\ 2 \overline{) 13} \quad \text{rem.} = 0 = a_1 \\ 2 \overline{) 6} \quad \text{rem.} = 0 = a_2 \\ 2 \overline{) 3} \quad \text{rem.} = 1 = a_3 \\ 2 \overline{) 1} \quad \text{rem.} = 1 = a_4 \\ 0 \quad \text{rem.} = 1 = a_5 \end{array}$$

$$53_{10} = 110101_2$$

Arithmetic Operation: Addition


- 和小時候學的直式加法差不多
- Binary number addition
- Example: $00011010 + 00001100 = ?$

00011010
 $+ 00001100$


 00100110

Carry (11 → 1 / → 00 or 01 or 10 → 0)

SUM (00 or 11 → 0 / → 01 or 10 → 1)

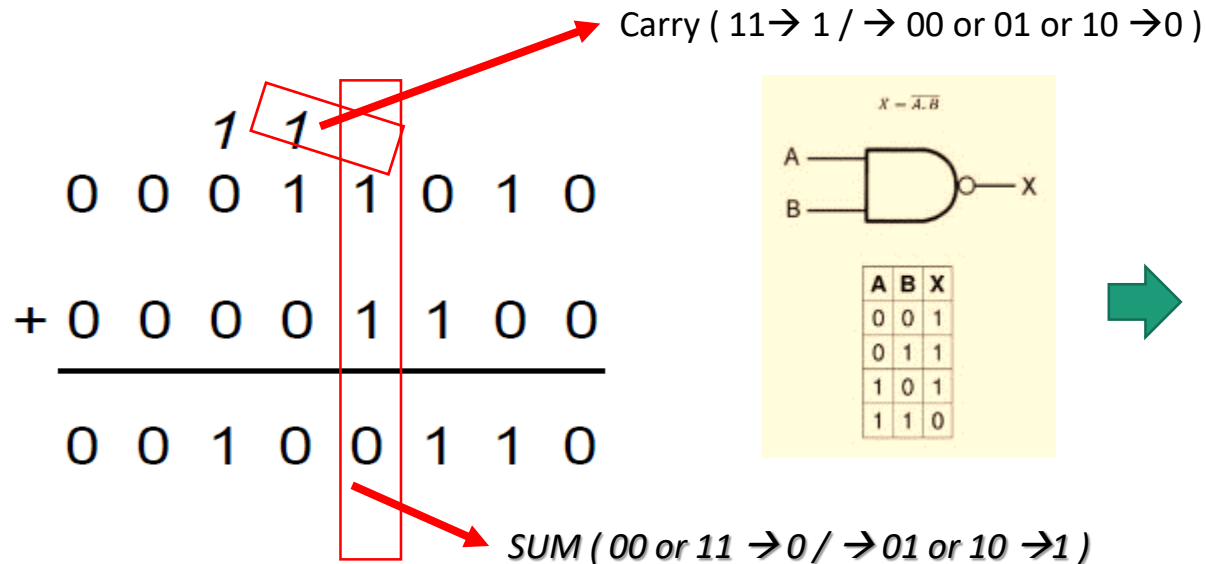


$x = \bar{A} \cdot \bar{B}$




A	B	X
0	0	1
0	1	1
1	0	1
1	1	0

One bit Adder

 

A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1



A	B	Out
0	0	0
0	1	1
1	0	1
1	1	0

Arithmetic Operation: Subtraction

- Binary number subtraction
- Example: $00100101 - 00010001 = ?$


$$\begin{array}{r}
 1 \\
 00100101 \\
 -00010001 \\
 \hline
 00010100
 \end{array}$$

$37 - 17 = 20$

How to simplify the calculation?




Gate level

 


A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1


Transistor level

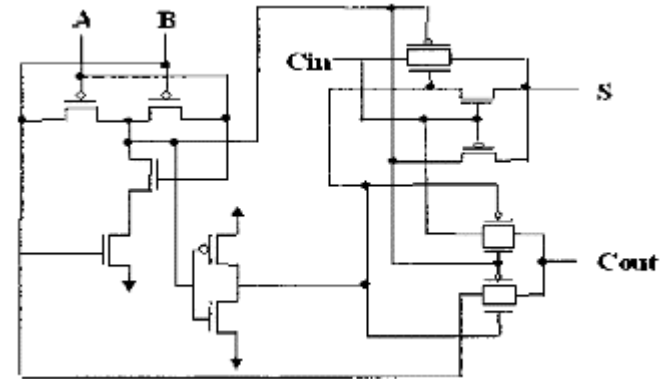


14 transistor 1-bit full adder

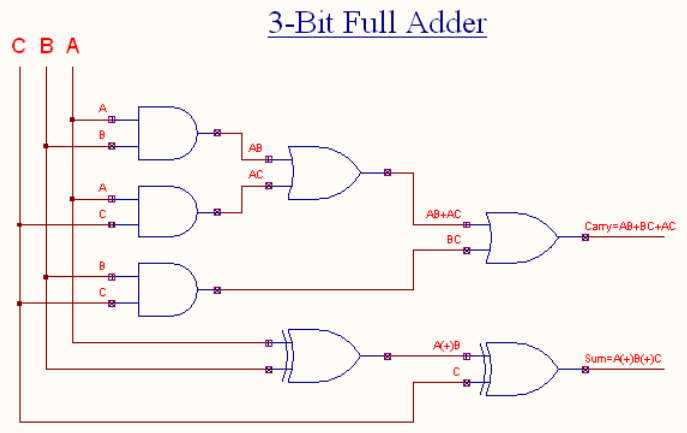

3-Bit Full Adder

 
 
$$\begin{array}{r}
 \\
 0 \ 0 \ 0 \ 1 \ 1 \ 0 \ 1 \ 0 \\
 + 0 \ 0 \ 0 \ 0 \ 1 \ 1 \ 0 \ 0 \\
 \hline
 0 \ 0 \ 1 \ 0 \ 0 \ 1 \ 1 \ 0
 \end{array}$$




4-digit Signed Binary Numbers

Decimal	Signed-2's complement
+7	0111
+6	0110
+5	0101
+4	0100
+3	0011
+2	0010
+1	0001
0	0000

Decimal	Signed-2's complement
-8	1000
-7	1001
-6	1010
-5	1011
-4	1100
-3	1101
-2	1110
-1	1111

Binary Information Processing

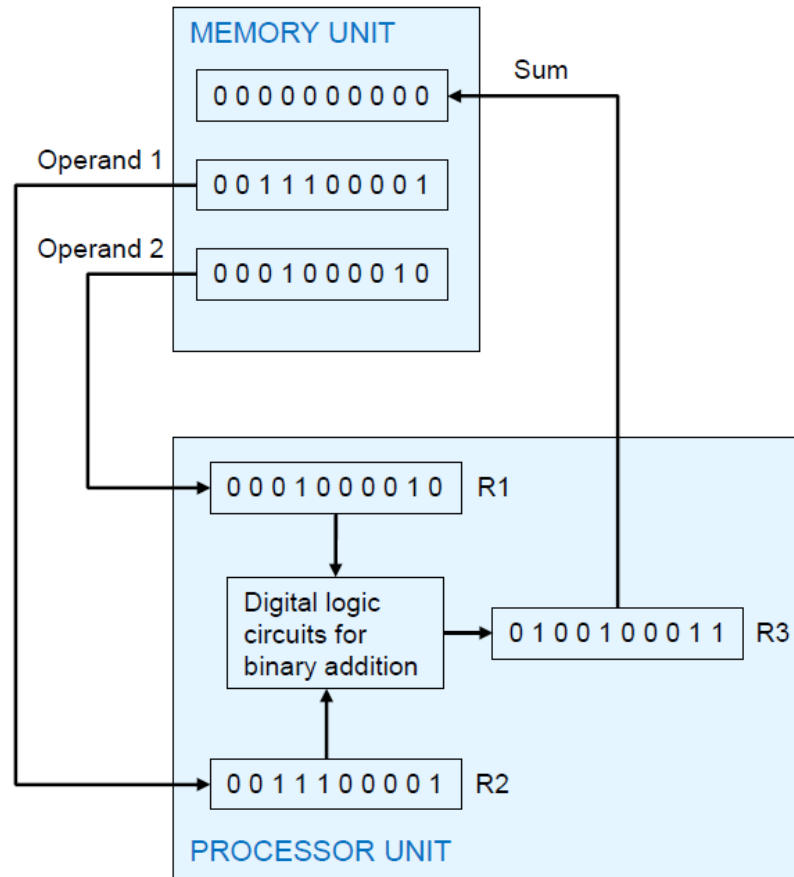



bit.ly/3B2rbmv